

Prepared by
Chandranayaka I R
Assistant Professor
Dept of ECE @GAT.

Module-4

DC-DC Converters



1. Introduction,
2. principle of step-down operation and it's analysis with RL load,
3. principle of step-up operation,
4. Step-up converter with a resistive load,
5. Performance parameters,
6. Converter classification,
7. Switching mode regulators: Buck regulator, Boost regulator, Buck-Boost Regulators,
8. Chopper circuit design.

Text Books:

1. Mohammad H Rashid, Power Electronics, Circuits, Devices and Applications, 3rd/4th Edition, Pearson Education Inc, 2014.

INTRODUCTION:

- * DC to DC Converter is also called as DC chopper which converts fixed DC voltage or fixed DC into variable DC.
- * A DC converter can be considered as a dc equivalent to an AC transformer with a continuously variable turns ratio.
- * The output voltage v_o can be greater or lesser than input hence chopper can be step up or step down type.
- * Choppers used in dc traction drives, trolley cars, marine lifts etc.

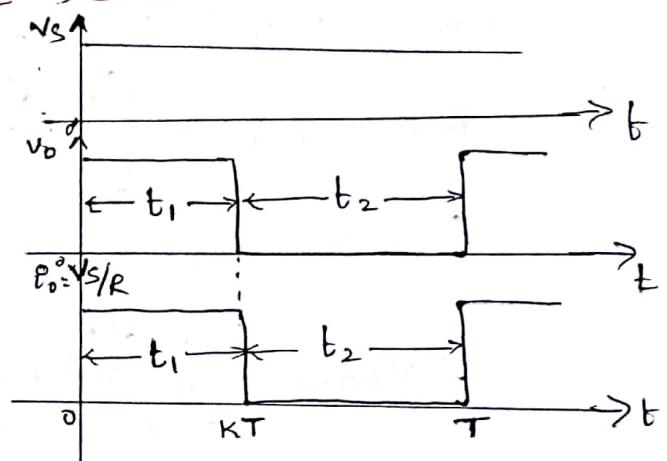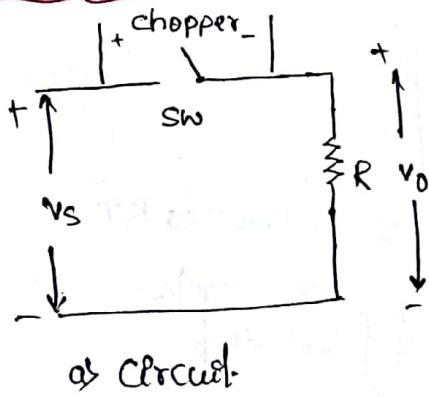PRINCIPLE OF STEP DOWN CHOPPER:

- * The above fig shows the circuit diagram of the basic step down chopper.
- * Switch is known as chopper can be implemented by using a power transistor, SCR, GTO, power MOSFET, IGBT.
- * When switch is closed for time t_1 , the input voltage v_s appears across the load ($v_o = v_s$)
- * When switch is open for time t_2 , the voltage across the load is zero.
- * practically switches have a finite voltage drop ranging from 0.5 to 2V.

Average output voltage:

$$V_{O(\text{avg})} = V_a = \frac{1}{T} \int_0^{t_1} V_o \cdot dt = \frac{1}{T} \int_0^{t_1} V_s \cdot dt$$

$$V_a = \frac{V_s}{T} [t]_0^{t_1} = \frac{V_s}{T} (t_1 - 0)$$

$$V_a = \frac{V_s \cdot t_1}{T} = \frac{V_s \cdot K}{T}$$

where
 $K = \frac{t_1}{T}$ = duty cycle of
chopper lies b/w 0 & 1

The avg load Currents

$$I_{Q(\text{avg})} = \frac{V_{O(\text{avg})}}{R} = \frac{V_s \cdot K}{R}$$

RMS output voltage:

$$V_o(\text{rms}) = \left[\frac{1}{T} \int_0^T V_o^2 dt \right]^{\frac{1}{2}}$$

from the waveform, $V_o = V_s$ from 0 to KT

$$\therefore V_o(\text{rms}) = \left[\frac{1}{T} \int_0^{t_1} V_s^2 dt \right]^{\frac{1}{2}} = \left[\frac{1}{T} \int_0^{KT} V_s^2 dt \right]^{\frac{1}{2}}$$
$$= \left[\frac{V_s^2}{T} \left[1 \right]_0^{KT} \right]^{\frac{1}{2}} = \left[\frac{V_s^2 \cdot KT}{T} \right]^{\frac{1}{2}}$$

$$V_o(\text{rms}) = \frac{V_s \cdot \sqrt{K}}{\sqrt{T}}$$

$$\text{RMS value of o/p Current is } I_o(\text{rms}) = \frac{V_o(\text{rms})}{R} = \frac{V_s \cdot \sqrt{K}}{R}$$

Input & output power of the chopper.

Input power (for lossless chopper)

Assume a lossless chopper, the input power to Chopper is same as output power since given by

$$P_I = \frac{1}{T} \int_0^{t_1} v_s i_s dt$$

$$i_s = \frac{v_s}{R}$$

$$= \frac{v_s \cdot v_s}{R \cdot T} \int_0^{KT} 1 \cdot dt$$

$$\therefore t_1 = KT$$

$$= \frac{v_s^2}{RT} [t]_0^{KT}$$

$$= \frac{v_s^2}{RT} (KT - 0)$$

$$= \frac{v_s^2}{RT} KT$$

$$P_I = P_o = K \cdot \frac{v_s^2}{R}$$

Output power (For lossless chopper)

$$P_o = \frac{1}{T} \int_0^{t_1} v_o i_o dt = \frac{1}{T} \int_0^{KT} v_o \cdot \frac{v_o}{R} dt$$

$$= \frac{v_o^2}{TR} \int_0^{KT} 1 dt = \frac{v_o^2}{RT} (KT - 0)$$

$$= \frac{v_o^2}{RT} \cdot KT$$

$$\therefore v_o = v_s$$

$$P_o = \frac{v_o^2}{R} \cdot K$$


Input & o/p power for Lossy chopper

If switching loss (V_{ch}) is considered then i/p power ps given by

$$P_p = \frac{1}{T} \int_0^{t_1} V_s \cdot I_s dt$$

$$= \frac{1}{T} \int_0^{KT} V_s \frac{(V_s - V_{ch})}{R} dt$$
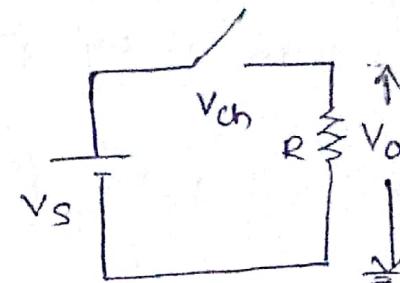
$$P_p = \frac{V_s \cdot (V_s - V_{ch}) \cdot K}{R}$$



$$V_o = V_s - V_{ch}$$


$$I = \frac{V_s - V_{ch}}{R}$$

Why o/p power is given by

$$P_o = \frac{1}{T} \int_0^{t_1} V_o \cdot I_o dt = \frac{1}{T} \int_0^{t_1} V_o \frac{V_o}{R} dt = \frac{K \cdot V_o^2}{R} \quad \because t_1 = KT$$


$$P_o = \frac{K \cdot (V_s - V_{ch})^2}{R}$$

Effective Input Resistance (R_i)

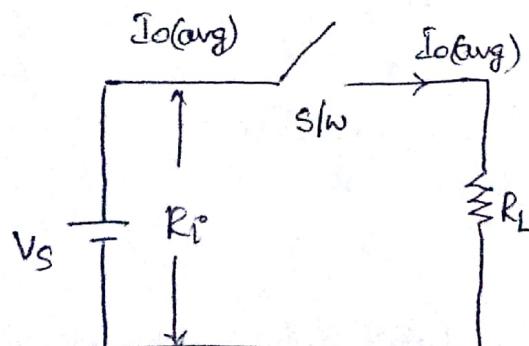

from the fig.
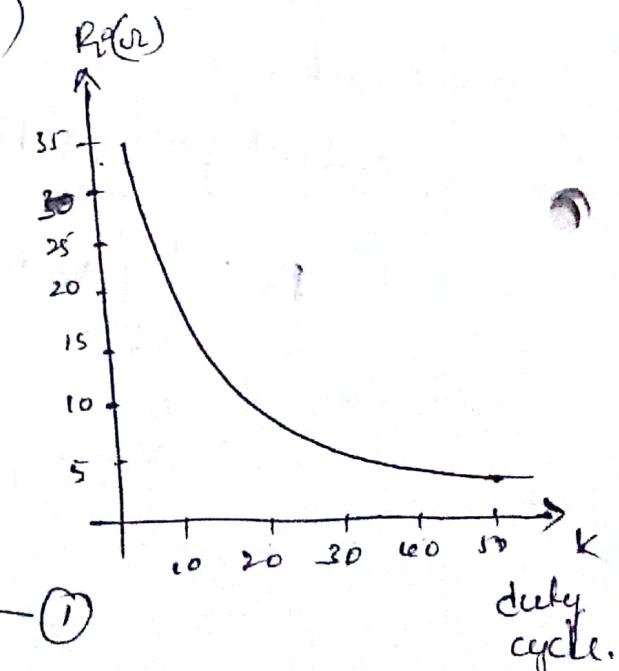
$$R_i = \frac{V_s}{I_o(\text{avg})} = \frac{V_s}{\frac{K \cdot V_s}{R}} = \frac{R}{K} \quad \text{--- (1)}$$



Eqn (1) indicates that the converter makes the i/p resistance R_i as variable resistance of R/K .


* the variation of normalized output resistance vs duty cycle is shown in above fig.

* Duty cycle η can be varied from 0 to 1 by varying t_1 .

* Output voltage V_o varied from 0 to V_s by controlling η & power flow can be controlled.

Chopper Control Techniques OR Time Ratio Control Techniques.


1- Constant frequency operation:

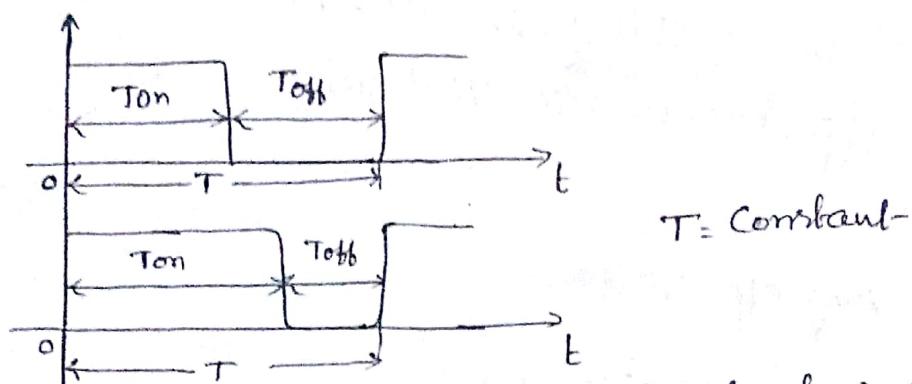

chopping frequency f is kept constant & on time is varied.

i.e. the width of pulse is varied this type of control is known as pulse width modulation (PWM).

2. Variable frequency operation.

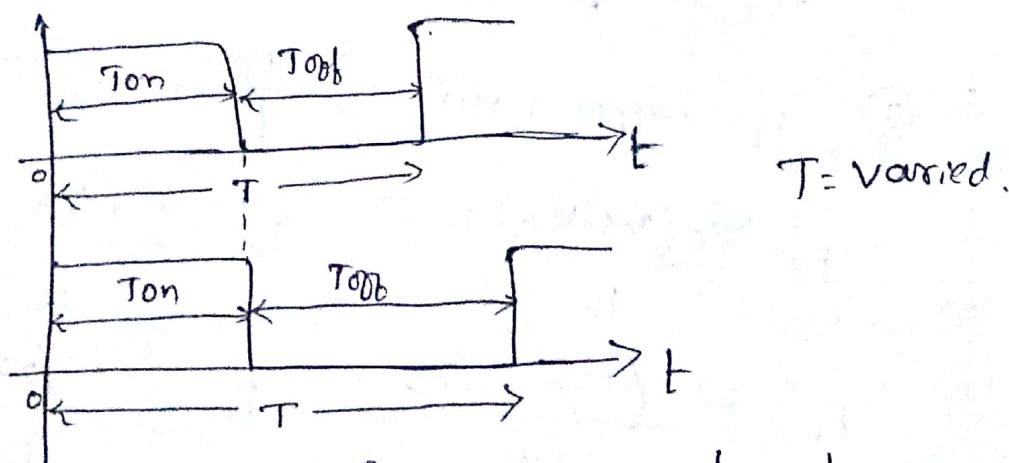

chopping frequency f is varied by keeping either T_{on} or T_{off} constant this is called frequency modulation.

Problems

- ① The DC chopper has a resistive load of $R = 10\Omega$, & the input voltage $V_S = 220V$ when chopper switch remains on its voltage drop is $V_{ch} = 2V$ chopping frequency is $f = 1\text{ kHz}$. If the duty cycle is 50%, determine
- the avg o/p voltage.
 - rms o/p voltage
 - chopper efficiency.
 - Effective i/p resistance R_i of the chopper
 - rms value of the fundamental component of o/p harmonic voltage.

Soluⁿ

Given data

$$R_L = 10\Omega$$

$$V_S = 220V$$

$$V_{ch} = 2V$$

$$f = 1\text{ kHz}$$

$$K = 50\% = 0.5$$

$$V_{avg} =$$

$$V_{rms} =$$

$$P_{in} = ?$$

$$\eta = ?$$

a) Avg o/p voltage.

$$V_a = K \cdot (V_S - V_{ch})$$

$$V_a = 0.5(220 - 2) = 109V$$

b) rms o/p voltage.

$$V_{rms} = \sqrt{K \cdot (V_S - V_{ch})}$$

$$V_{rms} = \sqrt{0.5} (220 - 2) = 154.15V$$

c) $\eta = \text{chopper efficiency} = \frac{P_o}{P_i} \times 100\%$

$$P_f = \frac{V_S(V_S - V_{ch})K}{R}, \quad P_o = \frac{K(V_S - V_{ch})^2}{R}$$

$$P_i = \frac{220(220 - 2)0.5}{10}, \quad P_o = \frac{0.5(220 - 2)^2}{10}$$

$$P_i = 2398W$$

$$P_o = 2376.2W$$

$$\eta = \frac{P_o}{P_i} = \frac{2376.2}{2398} \times 100 = 99.09\%$$

$$\textcircled{1} R_i = \frac{R}{K} = \frac{10}{0.5} = 20\Omega$$

\textcircled{2} o/p voltage v_o can be expressed in Fourier Series

$$v_o(t) = K \cdot v_s + \frac{v_s}{n\pi} \sum_{n=1}^{\infty} 8 \sin 2n\pi k \cos 2n\pi ft +$$

$$\frac{v_s}{n\pi} \sum_{m=1}^{\infty} (1 - \cos 2n\pi k) 8 \sin 2n\pi ft$$

fundamental component (for $n=1$) of o/p vtg harmonic
can be determined.

~~V(t)~~

$$v_i(t) = \frac{v_s}{\pi} \left[8 \sin 2\pi k \cos 2\pi ft + (1 - \cos 2\pi k) 8 \sin 2\pi ft \right]$$

$$= \frac{220 \times 2}{\pi} (\sin 2\pi \times 1000t)$$

$$= 140.06 \sin(6283.2t) \text{ & its rms value.}$$

$$V_r = 140.06 \sqrt{2} = 99.04V$$

\textcircled{2} A DC chopper has a resistive load of 20Ω & o/p voltage 220V when the chopper is on, its voltage drop is 1.5V & chopping freq is 10kHz . If the duty cycle is 80%. Determine the average o/p voltage, rms value of o/p voltage & chopper on time.

Sol:

Given data

$$\textcircled{1} v_o \text{ avg} = K(v_s - v_{ch})$$

$$= 0.8(220 - 1.5V) = 174.8V$$

$$v_s = 220V$$

$$v_{ch} = 1.5V$$

$$f = 10\text{kHz}$$

$$\textcircled{2} v_o(\text{rms}) = \sqrt{K} (v_s - v_{ch}) = \sqrt{0.8} (220 - 1.5) \quad K = 80\% = 0.8$$

$$\therefore = 195.43V$$

$$\textcircled{3} K = \frac{T_{on}}{T} = T_{on} \cdot f =$$

$$0.8 = T_{on} 10 \times 10^3 \quad T_{on} = 80 \mu\text{sec.}$$

Step-Down chopper with RL (RLB) Load.

- * choppers are used to drive the DC motors, moto, considered as RL (Inductive) Load.
- * Since the load is inductive, free wheeling diode D_m used in the circuit.
- * The operation of chopper can be divided into two modes, i.e mode 1 & mode 2.

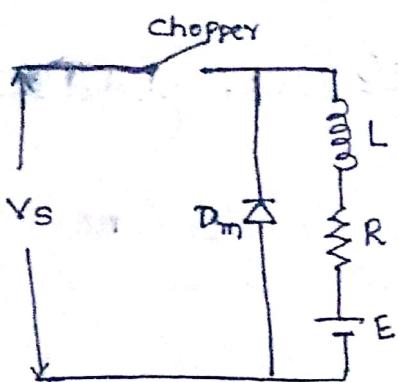


Fig1: Circuit diagram.


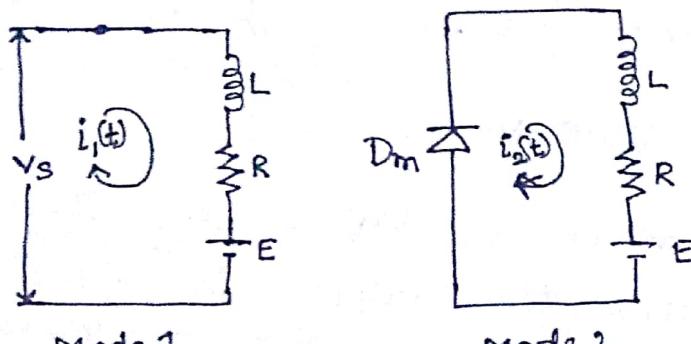


Fig2: Equivalent Circuits.

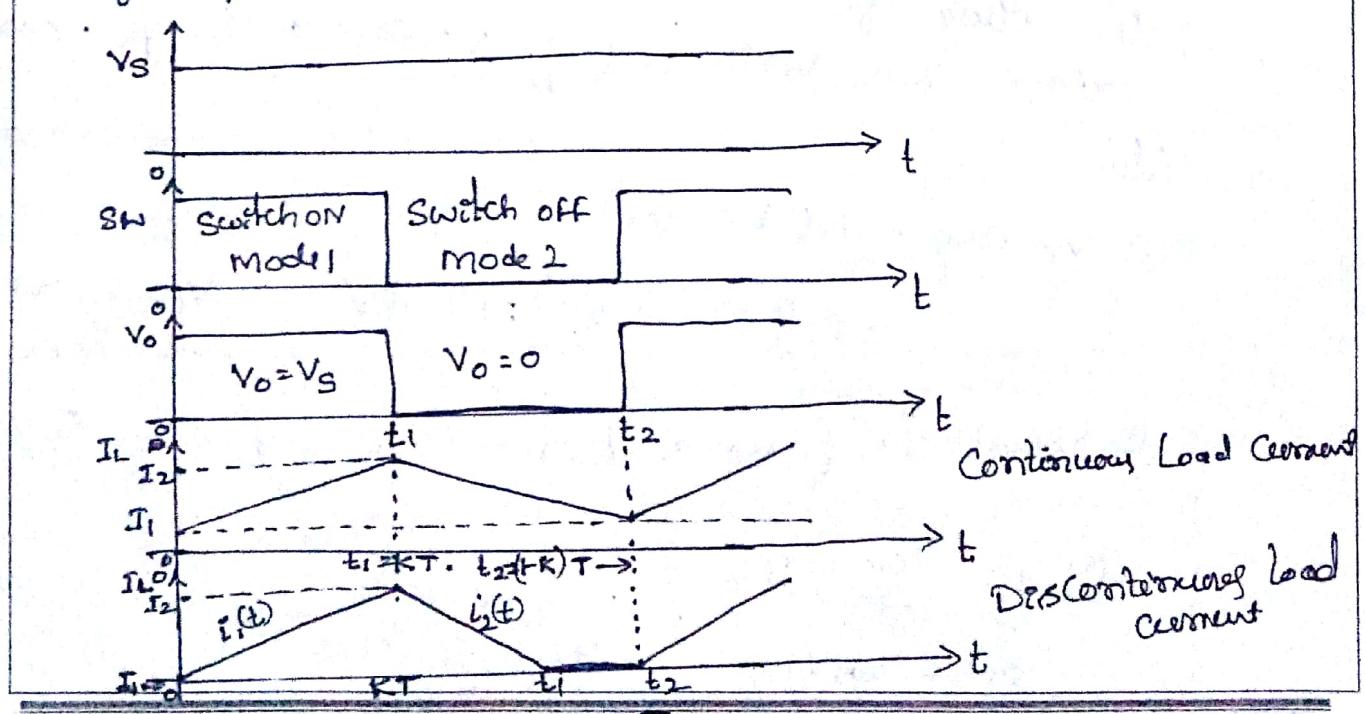

Continuous Load Current:

Mode 1: The switch is turned ON for $t = t_1 = KT$ where K = duty cycle, the o/p voltage is equal to the supply voltage i.e. $V_o = V_s$

The load current I_L in mode 1 is $i_L(t)$ changes between $I_{min} (= I_1)$ to $I_{max} (= I_2)$

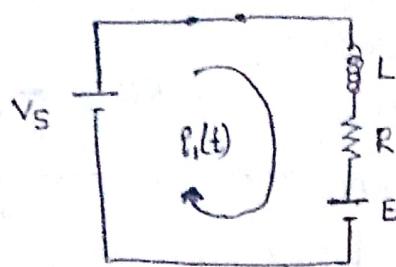


Fig 1

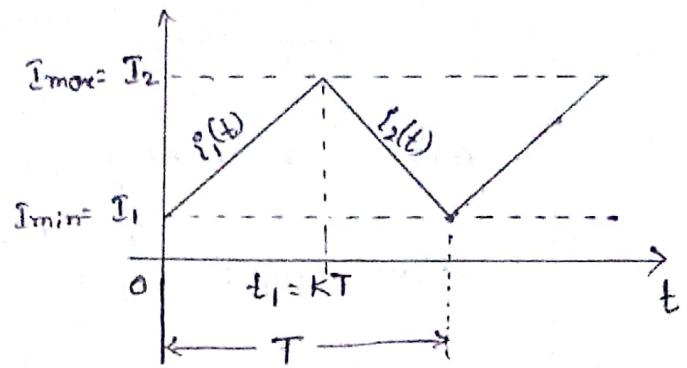


Fig 2.

Applying KVL to fig 1

$$V_s - L \frac{di_L(t)}{dt} - i_L(t)R - E = 0$$

$$V_s = L \frac{di_L(t)}{dt} + i_L(t)R + E \quad \text{--- (1)}$$

Taking Laplace transform & inverse Laplace transform of $\text{eqn } (1)$

$$i_L(t) = i_L(t=0) e^{-tR/L} + \frac{V_s - E}{R} \left[1 - e^{-tR/L} \right]$$

$$i_L(t=0) = I_1$$

$$t = t_1 = KT$$

at $t_1 = KT$

$$I_{max} = I_2 = I_1 e^{-KT/R} + \frac{V_s - E}{R} \left[1 - e^{-KT/R} \right]$$

Note: In mode 1 chopper is switched ON & current flows from Supply to load.

Mode 2:

Applying KVL to fig 2

$$0 = L \frac{di_2(t)}{dt} + i_2(t)R + E \quad \text{--- (2)}$$

Taking Laplace transform & inverse Laplace transform of $\text{eqn } (2)$

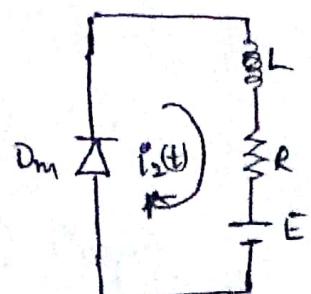


Fig (2)

$$I_2(t) = I_2 e^{-t R/L} - \frac{E}{R} [1 - e^{-t R/L}]$$

at $t_2 = (1-K)T$

$$I_{\text{min}} = I_1 = I_2 e^{-(1-K)T R/L} - \frac{E}{R} [1 - e^{-(1-K)T R/L}]$$

$$T = t_1 + t_2$$

$$T = KT + t_2$$

$$T - KT = t_2$$

$$-T(1-K) = t_2$$

$$\underline{t_2 = -T(1-K)}$$

peak to peak load current (or ripple current) can be obtained by.

$$\Delta I = I_{O(P-P)} = I_{\text{max}} - I_{\text{min}}$$


$$= I_2 - I_1$$

After Substituting $I_{\text{max}} (= I_2)$ & $I_{\text{min}} (= I_1)$.

$$\Delta I = I_{O(P-P)} = \frac{V_s}{R} \left[\frac{1 - e^{-KT R/L} + e^{-TR/L} - e^{-(1-K)T R/L}}{1 - e^{-TR/L}} \right]$$

Note: In mode 2 chopper is switched OFF & load current continues to flow through freewheeling diode Dm.

Discontinuous Load Current:

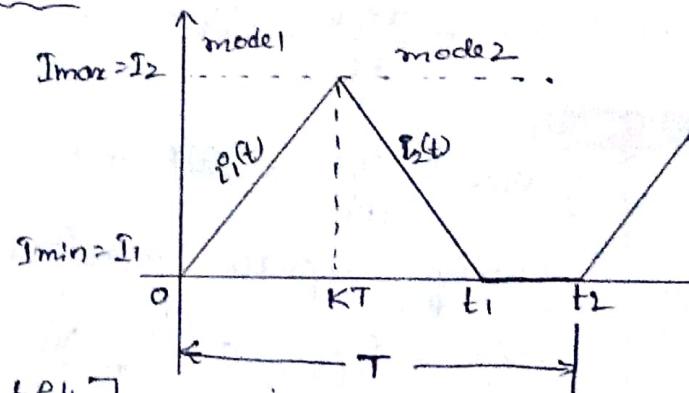

Mode 1:

$$I_1(t) = I_1 e^{-t R/L} + \frac{V_s - E}{R} [1 - e^{-t R/L}]$$

$$I_{\text{max}} = I_2 = \frac{V_s - E}{R} \left[1 - e^{-T R/L} \right] \quad \text{--- (1)}$$

Mode 2:

$$I_2(t) = I_2 e^{-t R/L} - \frac{E}{R}$$

$$\therefore 0 = I_2 e^{-t_1 R/L} - \frac{E}{R} \left[1 - e^{-t_1 R/L} \right] \quad \text{--- (2)}$$

Eqn (1) & (2) represents the discontinuous load current

- * To find the time t_1 at which load current becomes zero
Consider equation ② i.e.

$$0 = I_2 e^{-t_1 R/L} - \frac{E}{R} \left[1 - e^{-t_1 R/L} \right]$$

$$I_2 e^{-t_1 R/L} = \frac{E}{R} - \frac{E}{R} e^{-t_1 R/L}$$

$$e^{-t_1 R/L} \left[I_2 + \frac{E}{R} \right] = \frac{E}{R}$$

$$e^{-t_1 R/L} = \frac{\frac{E}{R}}{I_{max} + \frac{E}{R}}$$

$$I_2 = I_{max}$$

Taking ln on both sides.

$$-t_1 \frac{R}{L} = \ln \left[\frac{E/R}{I_{max} + E/R} \right]$$

$$t_1 \frac{R}{L} = -\ln \left[\frac{E/R}{I_{max} + E/R} \right]$$

$$t_1 = \frac{L}{R} \ln \left[\frac{I_{max} + E/R}{E/R} \right]$$

$$\therefore t_1 = \frac{L}{R} \ln \left[\frac{I_{max} R}{E} + 1 \right]$$

Problem.

- ① A chopper is feeding an RL load shown in fig. with $V_S = 220V$, $R = 5\Omega$, $L = 7.5mH$, $f = 1kHz$, $K = 0.5$ & $E = 20V$. Calculate.
- ② minimum instantaneous Load current (I_1)
 - ③ peak instantaneous current (I_2)
 - ④ maximum peak-to-peak load ripple current
 - ⑤ Avg value of load current I_0 .
 - ⑥ rms Load current I_0 .
 - ⑦ Effective input resistance R_i seen by source.
 - ⑧ rms chopper current I_R .

Solu:

Given data

$$V_S = 220V,$$

$$R = 5\Omega$$

$$L = 7.5mH$$

$$f = 1kHz$$

$$K = 0.5$$

$$a) I_{min} = I_{max} e^{-\frac{(1-K)TR/L}{R}} - \frac{E}{R} \left[1 - e^{-\frac{(1-K)TR/L}{R}} \right]$$

$$= I_{max} e^{-\frac{(1-0.5)5\Omega}{7.5mH \cdot 1kHz}}$$

$$\therefore \frac{1}{f} = T$$

$$I_{min} = 0.7165 I_{max} \quad (1)$$

$$I_{max} = I_{min} e^{-\frac{KTR/L}{R}} + \frac{V_S - E}{R} \left[1 - e^{-\frac{KTR/L}{R}} \right]$$


$$= I_{min} e^{-\frac{(0.5 \times 5)}{1k \times 7.5m}} + \frac{220}{5} \left[1 - e^{-\frac{(0.5 \times 5)}{1k \times 7.5m}} \right]$$

$$I_{max} = 0.7165 I_{min} + 12.4726 \quad (2)$$

Equn (1) in (2)

$$I_{max} = 0.7165 (0.7165 I_{max}) + 12.4726$$

$$= 25.63A$$

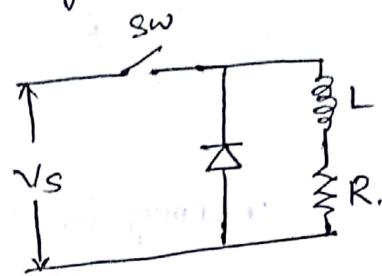

$$I_{min} = 0.7165(25.63)$$

$$I_{min} = 18.36 \text{ A}$$

$$(c) \Delta I = I_0(p-p) = I_{max} - I_{min} = 7.27 \text{ A}$$

$$\text{Let } I_0(\text{avg}) = \frac{I_{max} + I_{min}}{2} = \frac{25.63 + 18.36}{2} = 21.995 \text{ A.}$$

(e) rms load current

$$I_0(\text{rms}) = \left[I_{min}^2 + \frac{I_0(p-p)^2}{3} + I_0(p-p)I_{min} \right]^{\frac{1}{2}}$$

$$= \left[18.36^2 + \frac{(7.27)^2}{3} + (18.36 \times 7.27) \right]^{\frac{1}{2}}$$

$$I_0(\text{rms}) = 22.095 \text{ A}$$

$$(f) R_i = \frac{V_s}{I_0(\text{avg})} = \frac{V_s}{K I_0(\text{avg})} = \frac{220}{0.5(21.995)} = \frac{220}{11} = 20 \Omega$$

$$(g) I_T(\text{rms}) = \sqrt{K} \cdot I_0(\text{rms}) = \sqrt{0.5} (22.095) = 15.62 \text{ A.}$$

(2)

A chopper circuit shown. duty cycle = 0.5 & chopping frequency

$f = 5 \text{ kHz}$. Determine

i) min instantaneous load current.

ii) peak

current on load.

iii) p-p current on load.


iv) max (p-p) ripple current

v) Avg load current.

vi) rms load current.

vii) effective ip refrshance

Soluⁿ.

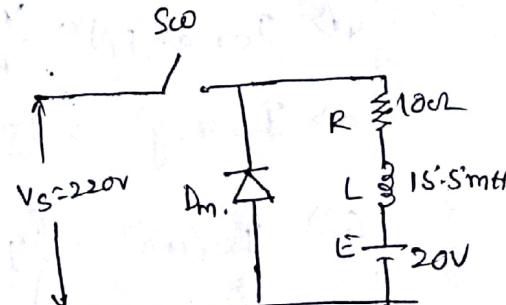

Given data

$$R = 10\Omega$$

$$L = 15.5 \text{ mH}$$

$$E = 20 \text{ V}$$

$$V_s = 220 \text{ V}$$

$$K = 0.5$$

$$f = 5 \text{ kHz}$$

W.K.T.

$$I_{max} = I_{min} e^{-KTR/L} + \frac{V_S - E}{R} \left[1 - e^{-KTR/L} \right]$$

$$\approx I_{min} e^{-\left(\frac{0.5 \times 10}{5k \times 15.5 \text{ mH}}\right)} + \left(\frac{220 - 20}{10} \right) \left[1 - e^{-\left(\frac{0.5 \times 10}{5k \times 15.5 \text{ mH}}\right)} \right]$$

$$I_{max} = 0.9375 I_{min} + 1.2495 \quad \text{--- (1)}$$

$$I_{min} = I_{max} e^{-(1-K)TR/L} - \frac{E}{R} \left[1 - e^{-(1-K)TR/L} \right]$$

$$I_{min} = 0.9375 I_{max} - 0.12496 \quad \text{--- (2)}$$

Substitute eqn (2) in (1)

(i) $I_{max} = 0.9375 (0.9375 I_{max} - 0.12496) + 1.2495$

$$I_{max} = 9.35 \text{ A}$$

(ii) Using eqn (2)

$$I_{min} = 0.9375 (9.35) - 0.12496$$

$$I_{min} = 8.642 \text{ A}$$

(iii) $I_{o(P.P.)} = \Delta I = I_{max} - I_{min} = 0.709 \text{ A}$

(iv) $I_{max(P-P)} = \frac{V_S}{R} \tanh\left(\frac{TR}{4L}\right) = \frac{220}{10} \tanh\left(\frac{10}{20k \times 15.5 \text{ mH}}\right) = 0.709 \text{ A}$

(v) $I_{o(\text{avg})} = \frac{I_{max} + I_{min}}{2} = \frac{9.35 + 8.642}{2} = 8.99 \approx 9 \text{ A}$



(vi) $I_{o(\text{rms})} = \sqrt{I_{min}^2 + \frac{I_{o(P.P.)}^2}{3} + I_{o(P.P.)} I_{min}}$

$$= \sqrt{(8.642)^2 + \left(\frac{0.709}{3}\right)^2 + (8.642 \times 0.709)} \text{ A}$$

$$I_{o(\text{rms})} = 8.99 \approx 9 \text{ A}$$

(vii) $R_o = \frac{V_S}{I_{o(\text{avg})}} = \frac{220}{K I_{o(\text{avg})}} = \frac{220}{0.5 \times 9}$

Principle of Step-up Chopper

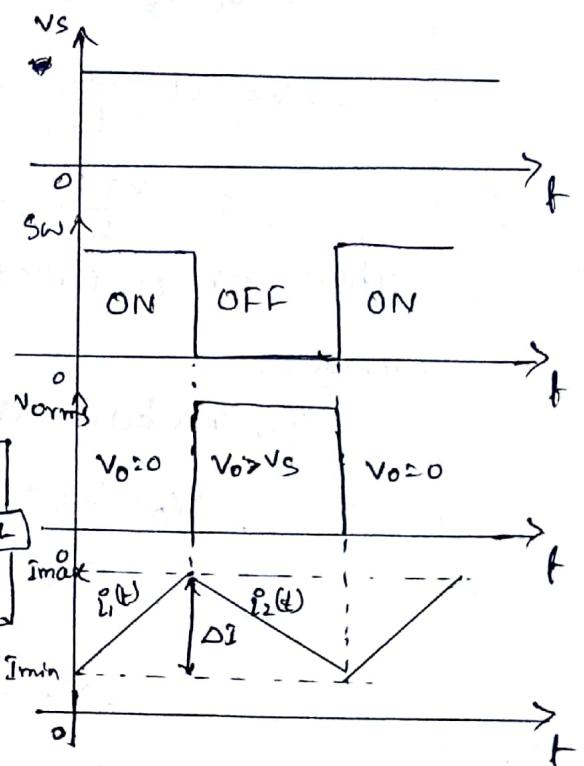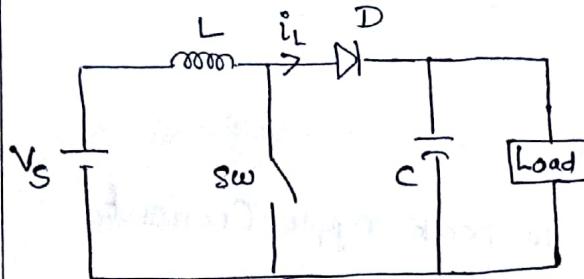

- * Here switch S_W is connected across the inductance & Supply.
- * capacitor C is used ac^c the load to make V_o smooth
- * The diode D blocks the flow of current to the load when switch S_W turned ON.

Mode 1: when the switch (chopper) is closed for time t_1 , the current flows through the inductance from the supply, the inductor current raises its energy is stored in the inductor 'L' ($V_L = v_s$) & off voltage is zero.

Mode 2: If the switch is opened at time t_2 , then the energy stored in the inductor is transformed to load through diode D (forward biased) & off voltage $V_o > v_s$ (i.e. $v_s + v_L$)

Output Voltage:

Model: when the chopper (S_W) is ON voltage across L is

$$V_L = L \cdot \frac{di(t)}{dt}$$

when $V_L = V_S$, $d\varphi(t) = \Delta I$, $dt = t_1$

$$\therefore V_S = L \cdot \frac{\Delta I}{t_1} \quad \text{--- (1)}$$

$$\Delta I = \frac{V_S \cdot t_1}{L} \quad \text{--- (2)}$$

where ΔI is called peak-to-peak ripple current.

mode 2:

Instantaneous o/p voltage is

$$V_O = V_S + V_L$$

$$= V_S + L \cdot \frac{d\varphi_2(t)}{dt}$$

$$= V_S + L \cdot \frac{\Delta I}{t_2} \quad \text{--- (3)}$$

equ'n (2) in (3)

$$V_O = V_S + K \cdot \frac{V_S t_1}{L t_2} \quad \text{N.K.T} \quad K = \frac{t_1}{t_1 + t_2}$$

$$= V_S \left(1 + \frac{t_1}{t_2} \right)$$

$$1 - K = 1 - \frac{t_1}{t_1 + t_2}$$

$$= V_S \left(\frac{t_2 + t_1}{t_2} \right)$$

$$1 - K = \frac{t_2 - t_1}{t_1 + t_2}$$

$$= V_S \left(\frac{1}{1 - K} \right)$$


$$1 - K = \frac{t_2}{t_1 + t_2}$$

$$V_O(\text{avg}) = \frac{V_S}{1 - K} \quad \frac{1}{1 - K} = \frac{t_1 + t_2}{t_2}$$

Load voltage depends on

deuty cycle
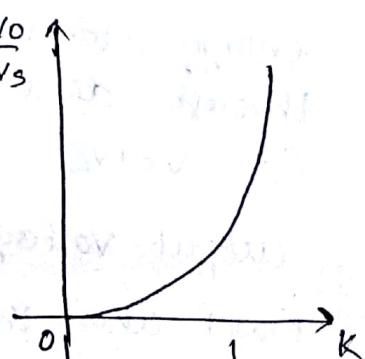
$$\text{for } K=0, V_O = V_S \quad \frac{V_O}{V_S} = 1$$



$$\text{for } K=1 \quad \frac{V_O}{V_S} = \infty$$

If a large Capacitor C_{PS} is connected a/c the load, the o/p voltage will be continuous & V_O would become equal to the average value.

Average output voltage:

Average voltage a/c inductor.

$$V_L = \frac{1}{T} \int_0^T V_L(t) dt = \frac{1}{T} \int_0^T L \cdot \frac{di_L(t)}{dt} dt = \frac{L}{T} \int_0^T dP_L(t).$$

above integration is w.r.t Inductance Current $dP_L(t)$
 \therefore limit changes.

$$\text{at } t=0 \quad P_L(t) = I_{\min}$$

$$\text{at } t=T \quad P_L(t) = I_{\max}$$

$$\therefore V_L = \frac{L}{T} \int_{I_{\min}}^{I_{\max}} dP_L(t) = \frac{L}{T} [P_L(t)]_{I_{\min}}^{I_{\max}} = \frac{L}{T} [I_{\max} - I_{\min}]$$

$$V_L = 0$$

The avg voltage across the inductance is zero.

Note: The inductor stores the energy when the switch is ON & supplies the energy to the load when the switch is OFF

* voltage across switch.

$$V_{AB} = \frac{1}{T} \int_0^T V_{AB}(t) dt$$

from kT to T , $V_{AB}(t) = V_o(\text{avg})$ & rest of the period it's '0'

$$\therefore V_{AB} = \frac{1}{T} \int_{kT}^T V_o(\text{avg}) dt$$

$$V_o = \frac{V_o(\text{avg})}{T} [1]_{kT}^T = \frac{V_o(\text{avg})}{T} [T - kT]$$


$$= \frac{V_o(\text{avg}) \cdot T}{T} [1 - k]$$

$$V_{AB} = V_o(\text{avg})(1 - k)$$

Applying KVL to the fig.

$$V_S - V_L - V_{AB} = 0$$

$$V_S = V_{AB} + V_L$$

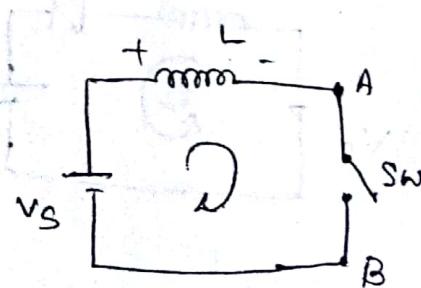


$$V_S = V_{O(\text{avg})} (1 - K) + 0$$



$$\therefore V_{O(\text{avg})} = \frac{V_S}{1 - K}$$

Use of Step up operation for energy transfer:

Principle of step up chopper can be applied to transfer energy from one voltage source to another.

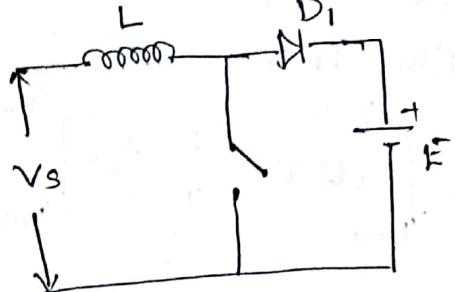

mode 1:

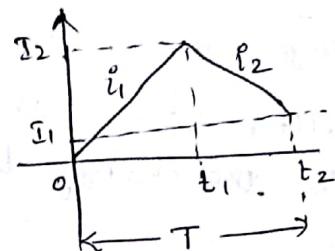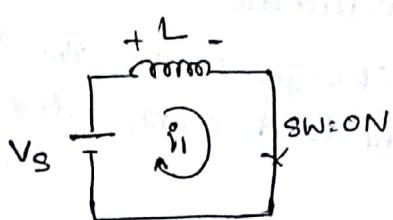

$$V_L = L \frac{di_1}{dt}$$


$$V_S \cdot dt = L \cdot di_1$$

$$i_1 = \frac{V_S \cdot t}{L} + I_1$$

where I_1 = Constant & Initial Current through inductor.
During model current should rise & necessary condition is

$$\frac{di_1}{dt} > 0 \quad \text{or} \quad V_S > 0.$$

mode 2:

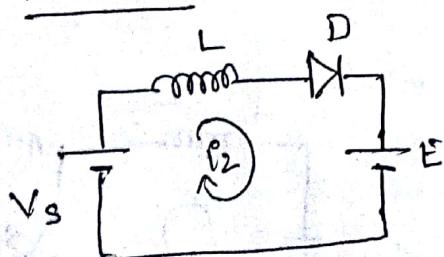

Applying KVL

$$V_S = L \frac{di_2}{dt} + E$$

$$V_S - E = L \frac{di_2}{dt}$$

$$di_2 = \left(\frac{V_S - E}{L} \right) dt$$

$\dot{I}_2 < 0$ is the Positive Current for mode 2
for stable system the current must fall & the necessary condition is

$$\frac{d\theta_2}{dt} < 0 \text{ or } V_S < E$$

∴ The condition for controllable power transfer is
 $0 < V_S < E$

$V_S < E$ to permit transfer of power from fixed or variable source to fixed dc voltage

when the chopper is turned ON energy is transferred from source V_S to L. If chopper is turned off energy stored in the inductor is forced to battery E.

Problem.

- ① A step up chopper has input voltage of 220V & output voltage of 660V. If the non-conducting time of the transistor chopper is 100μsec Compute the pulse width of output voltage in case peakwidth is halved, for constant frequency operation. Find new off voltage


Soln

Given data

$$V_O = 660V$$

$$V_S = 220V$$

$$t_{off} = 100\mu sec$$

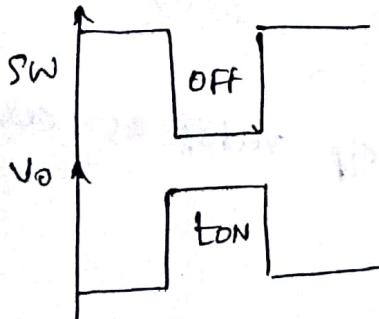

case 1) $t_{on} = ?$

$$\text{case 2)} T = \text{constant}, t_{on}' = \frac{t_{on}}{2}$$

$$V_O(\text{avg}) = ?$$

$$\text{Case i) } V_{\text{avg}} = \frac{V_s}{(1-K)}$$

$$660 = \frac{220}{1-K}$$

$$1-K = \frac{220}{660}$$

$$K = \frac{220}{660} = 0.33$$

$$K = \frac{t_{on}}{T} = \frac{t_{on}}{t_{on} + t_{off}}$$

$$t_{on} = K \cdot t_{off} + K \cdot T_{off}$$

$$t_{on}(1-K) = K \cdot T_{off}$$

$$t_{on} = \frac{K \cdot T_{off}}{1-K} = \frac{0.33 \cdot 100 \mu\text{s}}{1-0.33}$$

$$\therefore t_{on} = 200 \mu\text{s}$$

$$\text{Case ii) } T = \text{Const} = t_{on} + t_{off} = (100 + 200) \mu\text{s} = 300 \mu\text{s}$$

$$t_{on}' = \frac{200 \mu\text{s}}{2} = 100 \mu\text{s}$$

$$K = \frac{t_{on}}{T} = \frac{100 \mu\text{s}}{300 \mu\text{s}} = \frac{1}{3} = 0.33$$

$$V_{\text{avg}} = \frac{V_s}{1-K} = \frac{220}{1-0.33} = 330 \text{ V}$$

as t_{on} is halved, the d/c voltage is also reduced to half of its value.

Performance parameters:

The performance parameter of the chopper are as follows.

1. Duty cycle (k):

The duty cycle of the chopper controls its o/p voltage. The value of duty cycle lies b/w 0 & 1. Duty cycle can be controlled between a minⁿ value (k_{min}) & a maximum value (k_{max}) thereby limitation of minimum & maximum value of o/p voltage.

2. Chopping frequency or Switching frequency (f)

Frequency of the chopper is $f = \frac{1}{T}$, where T = period of o/p voltage waveform. The frequency should be as high as possible to reduce the load ripple current & minimize the size of series inductor in the load circuit.

3. operating speed of switch or devices.

Operating speed of the device depends on turn ON & turn OFF times of the switch. Hence switching frequency of the chopper depends on the speed of switching device.

Ex: MOSFET has very small turn on & turn off time hence it operates at very high speed.

Converter classification or chopper classification

Based on the direction of current & voltage flow.


Choppers can be classified as.

1. Class A choppers [First quadrant chopper] $[V_O = +ve, I_O = +ve]$
2. Class B choppers [Second quadrant chopper] $[V_O = +ve, I_O = -ve]$
3. Class C choppers [First & Second quadrant] $[I_O = +ve/-ve, V_O = +ve]$
4. Class D choppers [Third & fourth quadrant] $[V_O = +ve/-ve, I_O = +ve]$
5. Class E choppers [Four quadrant chopper] $[V_O = +ve/-ve, I_O = +ve/-ve]$

Class A Choppers:

In class A both output voltage & load current are positive. This is called as I quadrant chopper. It is said to be operated as rectifier.

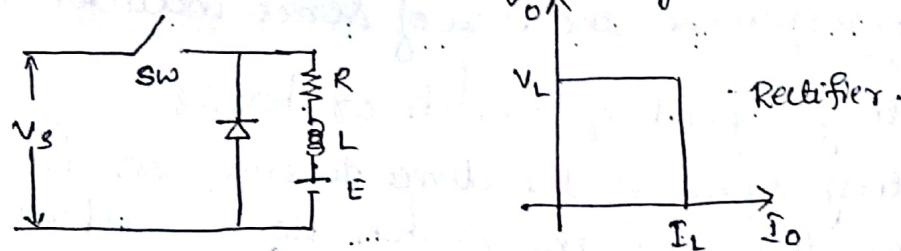Step down chopper is basically class A chopper.




$I_o = I_L = +ve$ at V_o flowing from Source to Load.

Class B Chopper:

In class B load voltage is +ve & current is -ve if flows from load to source.

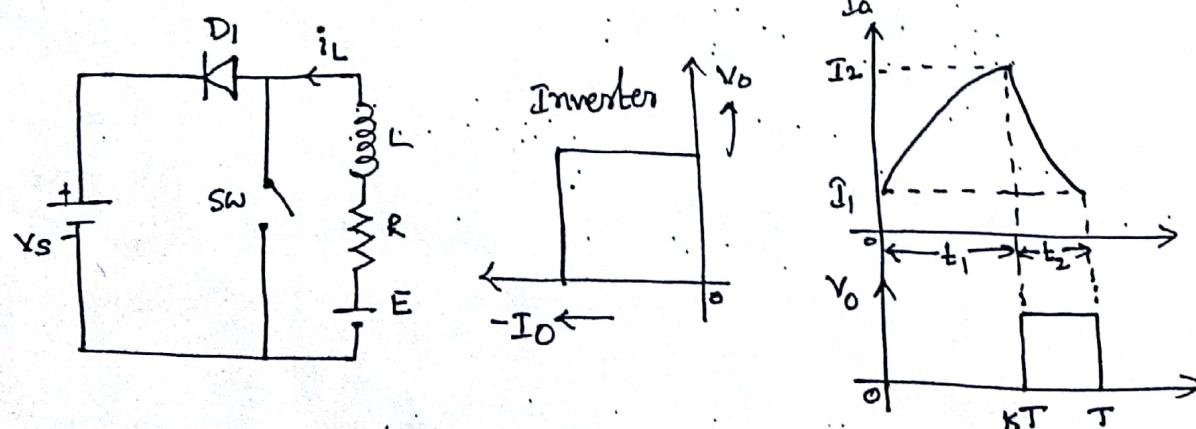Class B is said to be operated as an inverter.



In Class B, load voltage is positive & current is -ve & flows from load to source.

Class B is said to be operated as an inverter.

operation:

When chopper is ON, the voltage E drives the current through inductor L & store energy in L & Load voltage $V_L = 0$.

Load current is given by.

$$0 = L \frac{di}{dt} + R i_L + E \quad \text{--- (1)}$$

$$\text{i.e., } i_L(t) = I_1 e^{-t/R/L} - \frac{E}{R} [1 - e^{-t/R/L}] \quad \text{--- (2)}$$

The above eqn is valid for $0 \leq t \leq t_1 [= KT]$
At time $t = t_1 = KT$, load current I_L becomes

$$I_L = I_2 \text{ at } t = t_1 = KT$$


when chopper is OFF

In this mode, load current falls &
is given by

$$V_S = L \frac{di_L}{dt} + R i_L + E$$

$$\therefore i_L(t) = I_2 e^{-t/R/L} + \frac{V_S - E}{R} [1 - e^{-t/R/L}]$$

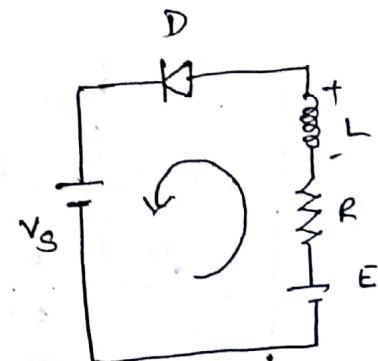
This is valid for $0 \leq t \leq t_2$ where $t_2 = (1-K)T$



Class C Choppers:

In this chopper load current is either +ve or -ve & load voltage is always +ve, this is known as two quadrant chopper.

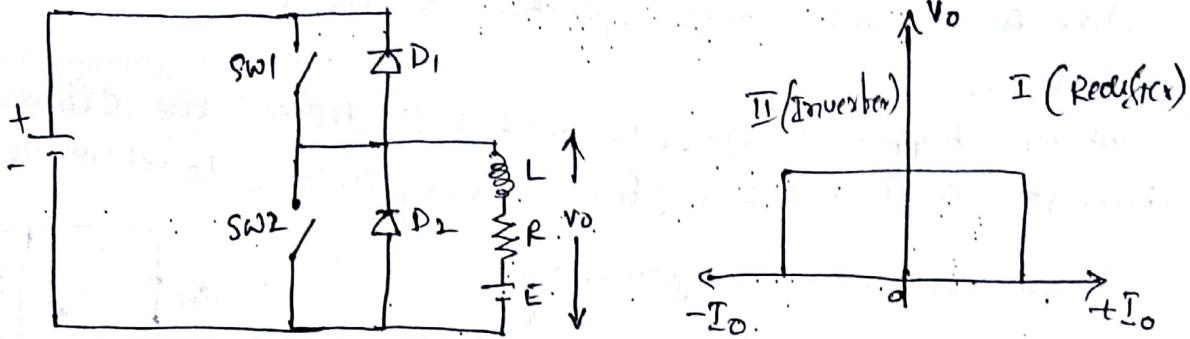Class A & Class B are combined to form class C chopper.



operation

- * For I quadrant operation $S_1 \& D_1$ operate & $S_2 \& D_2$ does not conduct.
- * When SW_1 is turned ON, DC supply gets connected to the load & $V_o = +V_s = +ve$.
- * Current flows from source to load $\therefore I_o = +ve$

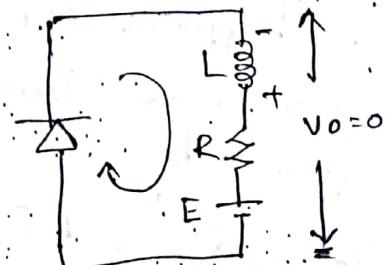
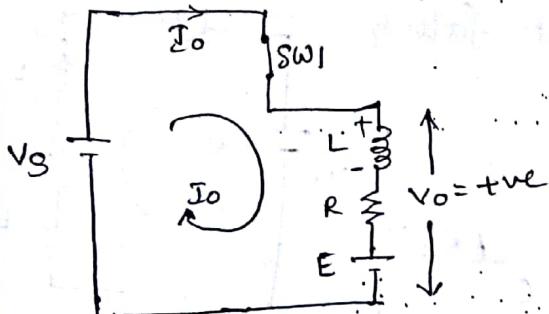


fig ⑥

fig ⑤
When switch S_1 is off - free wheeling action takes place through diode D_2 as shown in fig ⑥. Thus load voltage is zero & current is +ve.

- * For II quadrant operation $S_2 \& D_2$ conduct.

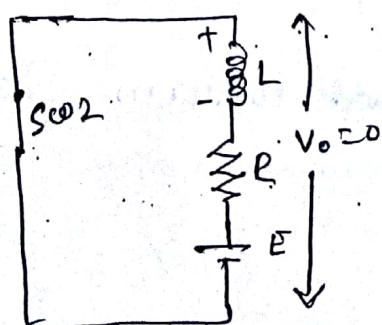


fig ⑤

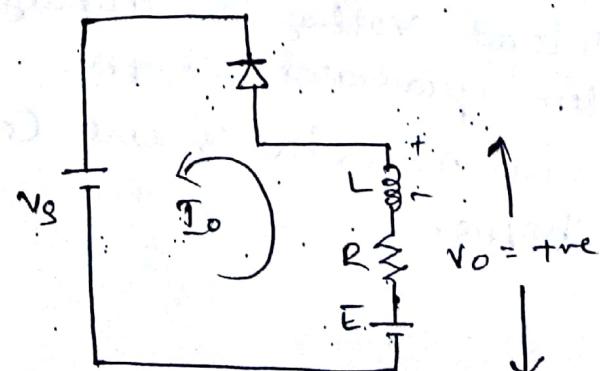


fig ⑥



S_{CO2} Conducts. Inductor stores energy from source E & free wheeling action backplate & $V_o = 0$ & $I_o = -ve$. flows from load.

When S_{CO2} is turned off, induced emf in the inductor forces D_1 to conduct & stored energy is returned back. the load voltage is +ve & current I_o is -ve as it is flowing from load to source.

In II quadrant operated as Regenerative breaking or converter.

Class D choppers:

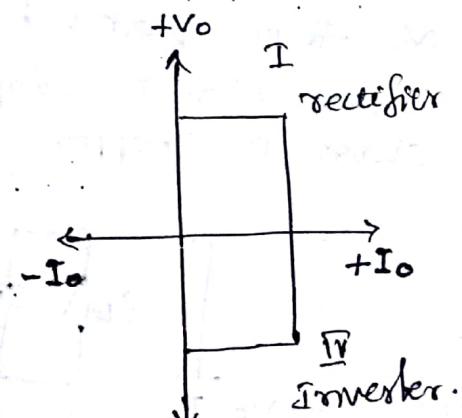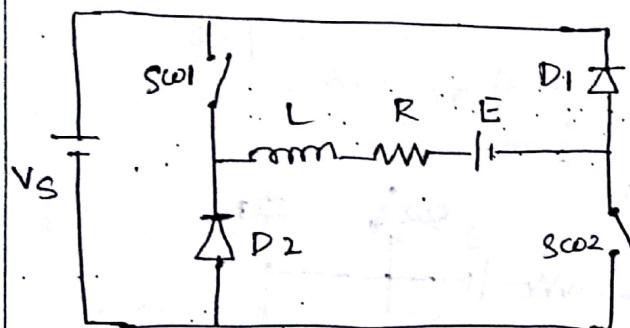In Class D Chopper, load voltage is +ve & load current is always +ve. It operates as rectifier or inverter.



when both switches are turned ON, the o/p voltage $V_o = +V_s$ & load current is +ve as shown in fig(i) & inductor stores energy.

when both switches are turned off, induced emf.

of inductor forces D_1 & D_2 to conduct [L releases the energy stored]. So the diode provide path for a load current & it is maintained in the same direction

$I_o = +ve$ & load voltage = -ve shown by fig (ii).

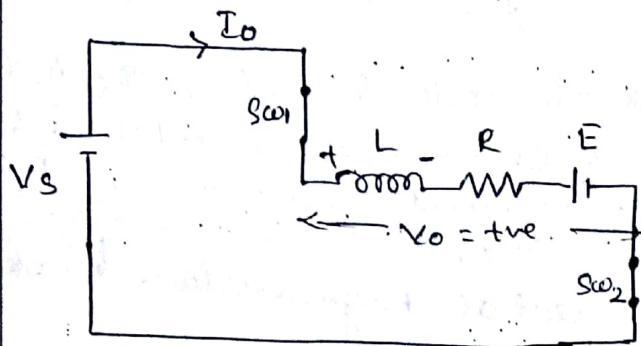


Fig (i)


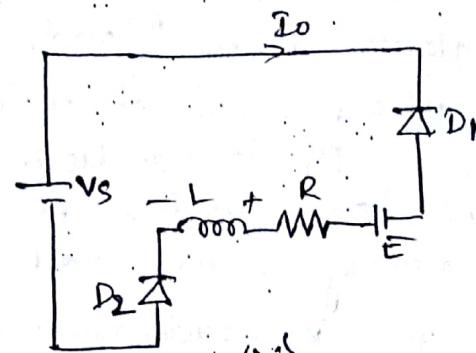
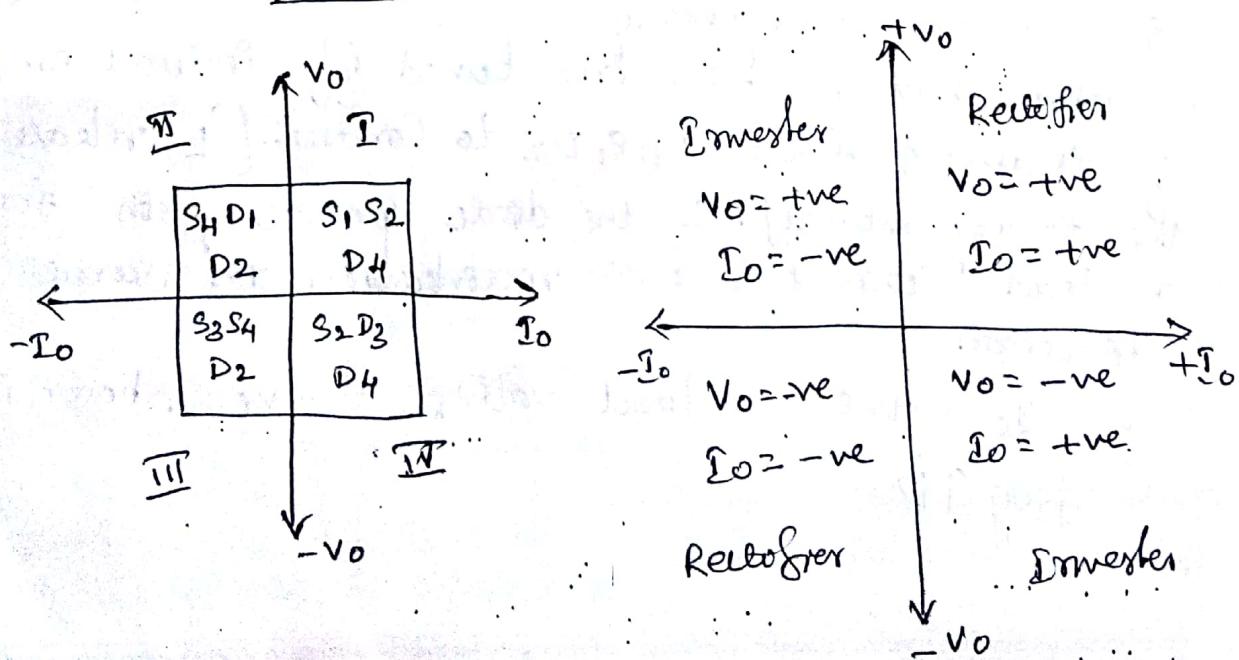


Fig (ii)

Class E operation:


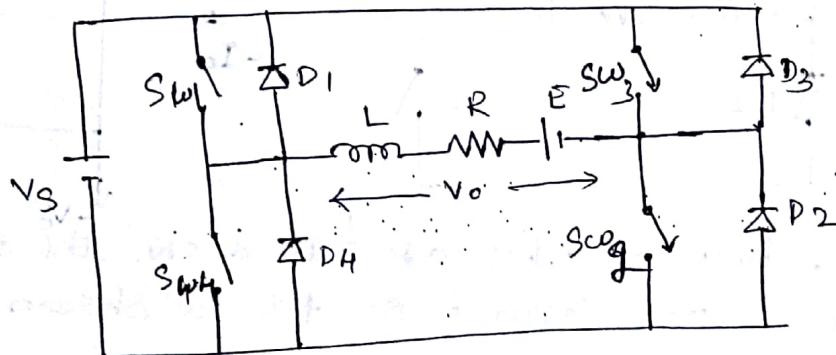
- * In class E chopper, Load current is either +ve or -ve & load voltage is also either +ve or -ve this is known as four quadrant chopper.
- * Two class C choppers can be combined to form a class E chopper.




I quadrant operation:

- * To operate on 1st quadrant s_{o1} & s_{o2} is turned ON, s_3 & s_4 is off. Then current flows from source to load. $\therefore I_o = +ve$ & $V_o = +ve$ ($V_s - s_{o1} - L - R - E - s_2$)
 - * When s_{o1} is turned off, current flows through $(L - R - E - s_2 - D_4)$, free wheeling action takes place.
- $V_o = 0$ & $I_o = +ve$.

- * When both the switches are turned off, stored energy in the inductor ($-imm+$) forces current through D_3 & D_4 ($L - R - E - D_3 - V_s - D_4$) since current maintained in same direction.

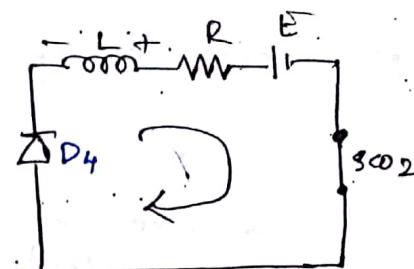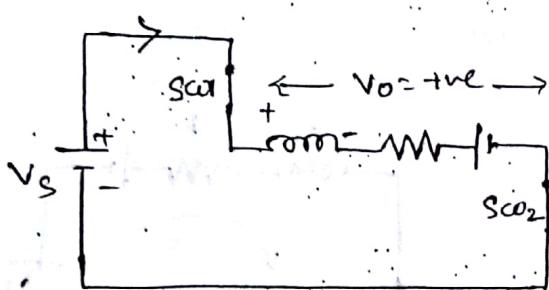
IV quadrant operation:

To ps +ve & V_o is -ve \therefore chopper is operating on IV quadrant.

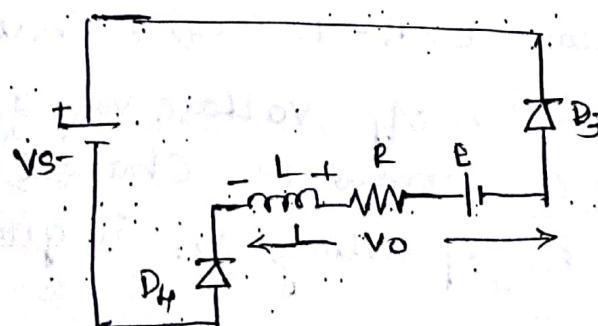
II Quadrant operation:

When s_{o3} is turned off, current flows on the paths ($L - T_4 - D_2 - E - R$) & freewheeling action ($-imm-$) takes place & $V_o = 0$ & $I_o = -ve$

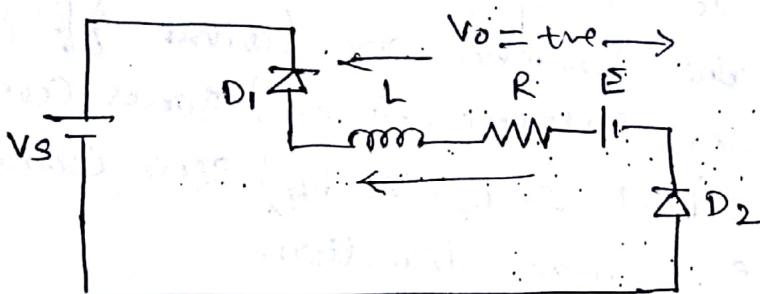- * Now when S_4 is also turned off - energy stored in inductor (Im^+) flows current through D_1 & D_2 (i.e. $L - D_1 - V_S - D_2 - E - R$)
- Current flows through supply, thus current is $I_o = -ve$ & $V_o = +ve$ \therefore Chopper operating as II quadrant.



III Quadrant operation.

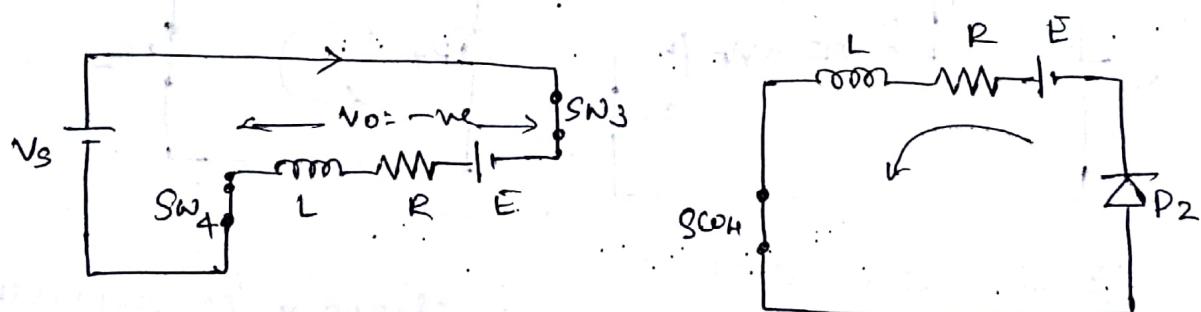

To reverse the direction of rotation of motor ($E = -ve$) when S_{CO3} & S_{CO4} is turned ON, current flows ($V_S - S_{CO3} - E - R - L - S_{CO4}$) & inductor stores energy (Im^+). Output voltage V_o & I_o is $-ve$ (\because direction of current is changed). \therefore Chopper is operating in III quadrant.

Note:

A quadrant chopper has the capability to operate in all the four quadrants.

Switching Mode Regulators:

DC choppers can be used as switching mode regulators to convert a dc voltage i.e unregulated to a regulated dc output voltage.

Regulation is achieved by pulse width modulation at a fixed frequency and the switching device is normally power BJT, MOSFET or IGBT.

Different types of dc-dc converters are

- 1. Buck (step-down) converter
- 2. Boost (Step-up) converter
- 3. Buck-Boost (stepdown-up) converter
- 4. Cuk converter

* Buck-Boost and Cuk converters are the combination of Step-down and Step-up converter.


1. Buck Converters or Regulators:

In buck regulator avg output voltage is less than the input voltage V_s . Hence the name buck.


Circuit diagram is as shown in the figure.

* By varying the duty cycle K of the switch, the average o/p voltage can be controlled.


* very popular regulator

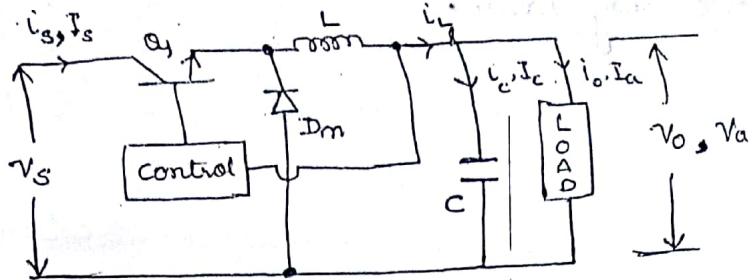

mode 1

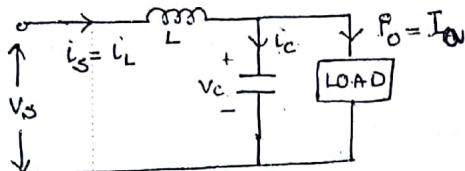

mode 2

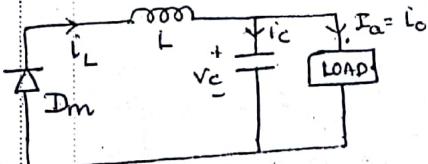


The circuit operation can be divided into two modes.

mode 1 begins when transistor Q_1 is switched ON at $t=0$.

The input current which increases flows through L , C and load resistor R .

mode 2 begins when transistor Q_1 is switched off at $t=t_1$. The free-wheeling diode D_m conducts due to energy stored in the inductor and current continues to flow through L , C and D_m .

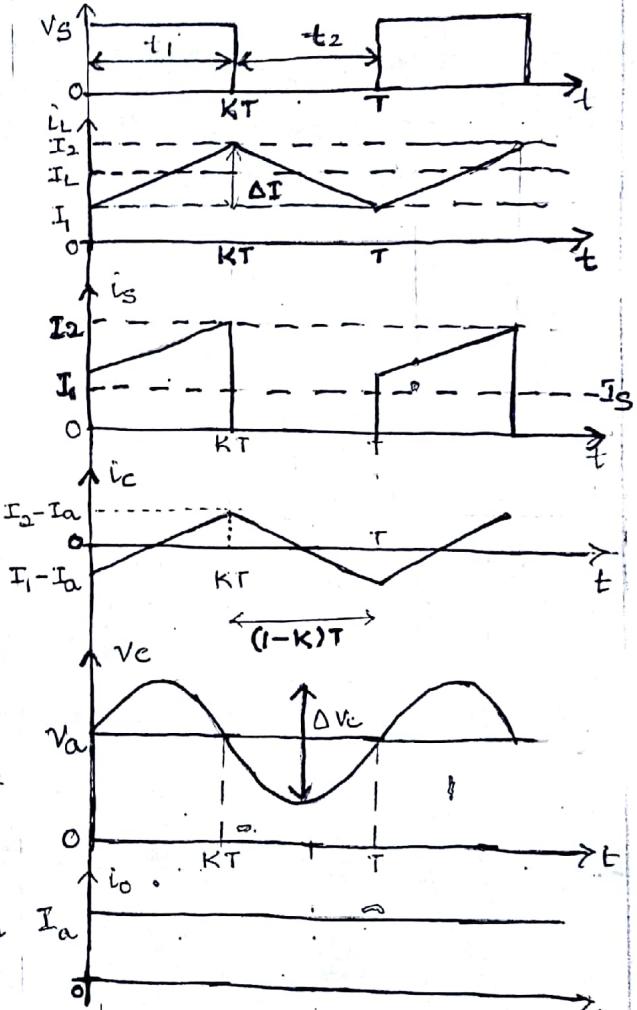Inductor current falls until Q_1 is switched on again in the next cycle.



Voltage across the inductor L is

$$V_L = L \cdot \frac{di}{dt}$$

when current rises linearly from I_1 to I_2 in time t_1 ,

$$V_s - V_a = L \cdot \frac{(I_2 - I_1)}{t_1} = L \cdot \frac{\Delta I}{t_1}$$

$$\Rightarrow t_1 = \frac{\Delta I \cdot L}{V_s - V_a} \quad \& \quad \Delta I = \frac{(V_s - V_a)t_1}{L} \rightarrow \textcircled{1}$$

at time t_2 , the inductor current falls linearly from I_2 to I_1 ,

$$-V_a = -L \cdot \frac{\Delta I}{t_2}$$

$$\Rightarrow t_2 = \frac{\Delta I \cdot L}{V_a} \quad \& \quad \Delta I = \frac{V_a t_2}{L} \rightarrow \textcircled{2}$$

Equating eqⁿ ① and eqⁿ ②

$$\Delta I = \frac{(V_s - V_a)t_1}{L} = \frac{V_a \cdot t_2}{L}$$

$$V_s t_1 - V_a t_1 = V_a \cdot t_2$$

$$V_a(t_1 + t_2) = V_s(t_1)$$

$$V_a = V_s \left(\frac{t_1}{t_1 + t_2} \right)$$

$$V_a = V_s \cdot K \rightarrow \textcircled{3} \quad \text{where } K = \frac{t_1}{t_1 + t_2} = \text{duty cycle}$$

Assuming a lossless circuit,

$$V_s I_s = V_a I_a = K \cdot V_s \cdot I_a$$

and average input current $I_s = K \cdot I_a$

* Switching period T can be written as

$$T = t_1 + t_2 = \frac{\Delta I \cdot L}{V_s - V_a} + \frac{\Delta I \cdot L}{V_a} = \frac{\Delta I \cdot L \cdot V_s}{V_a(V_s - V_a)} \rightarrow \textcircled{4}$$

$$\frac{1}{f} = \frac{\Delta I \cdot L \cdot V_s}{V_a(V_s - V_a)} \rightarrow (5)$$

∴ peak to peak ripple current of inductor

$$\Delta I = \frac{V_a(V_s - V_a)}{f \cdot L \cdot V_s} = \frac{V_a \left(\frac{V_s}{V_s} - \frac{V_a}{V_s} \right)}{f \cdot L}$$

$$\Delta I = \frac{V_a (1 - K)}{f \cdot L} = \frac{K \cdot V_s (1 - K)}{f \cdot L} \rightarrow (6)$$

Using $\$CL$, inductor current can be written as

$$i_L = i_c + i_o \rightarrow (7)$$

if we assume that load ripple current Δi_o is very small and negligible $\Delta i_L = \Delta i_c \rightarrow (8)$

* average capacitor current which flows into for $\frac{t_1}{2} + \frac{t_2}{2} = \frac{T}{2}$

$$I_c = \frac{\Delta I}{4} \rightarrow (9)$$

* The capacitor voltage is expressed as

$$V_c = \frac{1}{C} \int i_c dt + V_c(t=0) \rightarrow (10)$$

P-P voltage of capacitor is

$$\Delta V_c = V_c - V_c(t=0) = \frac{1}{C} \int i_c dt + V_c(t=0) - V_c(t=0)$$

$$\Delta V_c = \frac{1}{C} \int_0^{T/2} \frac{\Delta I}{4} dt = \frac{\Delta I T}{8C} = \frac{\Delta I}{8fC} \rightarrow (11)$$

Substituting eq (6) in (11)

$$\Delta V_c = \frac{V_a (V_s - V_a)}{8LC f^2 V_s}$$

or

$$\Delta V_c = \frac{V_s \cdot K (1 - K)}{8 \cdot f^2 \cdot LC}$$

* Condition for Continuous inductor current. If I_L is avg inductor current then $\Delta I = 2 I_L = 2 i_o$

$$\frac{V_s (1 - K) \cdot K}{f \cdot L} = 2 \cdot K \cdot V_s$$

$$L_C = L = \frac{R (1 - K)^2}{2 f} \quad (L_C > \text{critical value})$$

Now Avg capacitor voltage $\Delta V_c = 2 V_o$

$$\frac{V_s K (1 - K)}{8 L C f^2} = 2 \cdot K \cdot V_s$$

$$C_C = C = \frac{(1 - K)}{16 f^2 L}$$

- * Since the buck regulator requires only one transistor it is simple and has high efficiency greater than 90%.
- * The inductor L limits the $\frac{di}{dt}$ of the load current.
- * The i/p current is discontinuous and a smoothing i/p filter is required.
- * It provides one polarity of output voltage and unidirectional output current. It requires a protection circuit in case of possible short circuit across the diode path.

Problem

The buck regulator has an input voltage of $V_S = 12V$. The required output voltage is $V_a = 5V$, $R = 50\Omega$ and peak to peak output ripple voltage is $20mV$. The switching frequency is $25KHz$. If the peak to peak ripple current of inductor is limited to $0.8A$, determine

- a) duty cycle K
- b) filter inductance L
- c) filter capacitor C
- d) critical value of $L \& C$

Soln Given $V_S = 12V$, $V_a = 5V$, $\Delta V_C = 20mV$, $f = 25KHz$, $\Delta I = 0.8A$

$$a) V_a = K \cdot V_S \Rightarrow K = \frac{V_a}{V_S} = \frac{5}{12} = 0.4167 = 41.67\%$$

$$b) \Delta I = \frac{V_S K (1-K)}{f L}$$

$$L = \frac{V_S K (1-K)}{f \cdot \Delta I} = \frac{12 \times 0.41 \times (1-0.41)}{25K (0.8A)} = 145.83 \mu H$$

$$c) \Delta V_C = \frac{\Delta I}{8 f C}$$

$$C = \frac{\Delta I}{8 f \Delta V_C} = \frac{0.8}{8(25K) 20mV} = 200 \mu F$$

$$d) L_C = L \cdot \frac{(1-K)R}{2f} = \frac{(1-0.4167) 500}{2 \times 25 \times 10^3} = 5.83mH, C_C = \frac{1-K}{16L \cdot f^2} = 0.404 \mu F$$

Given data

$$V_S = 12V$$

$$V_a = 5V$$

$$\Delta V_C = 20mV$$

$$f = 25KHz$$

$$\Delta I = 0.8A$$

$$K = ?$$

$$L = ?$$

$$C = ?$$

$$R = 50\Omega$$

Boost Regulators

- * In a boost regulator, the output voltage is greater than the input voltage - hence the name 'boost'.
- * A boost regulator using a power MOSFET is shown in fig and is similar to a step-up chopper.

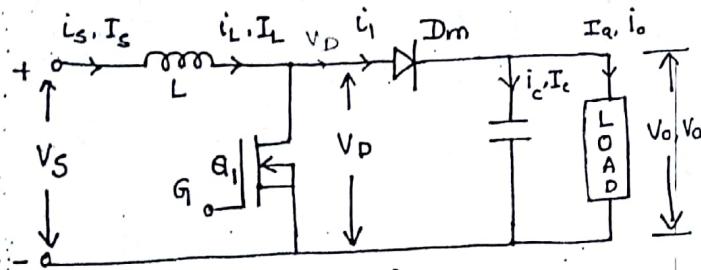


fig :- circuit diagram

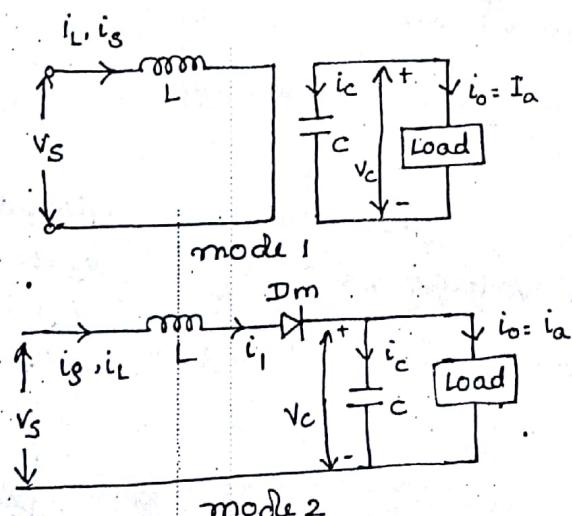


fig : Equivalent Circuits

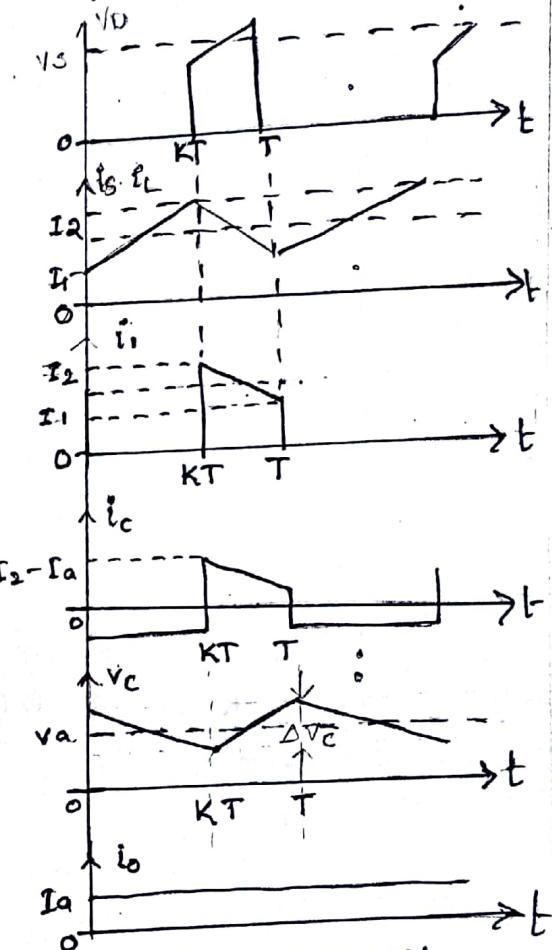


fig : waveforms

- * The circuit operation can be divided into two modes.
- (*) mode 1 begins when transistor Q_1 is switched on at $t=0$. The input current, which rises, flows through inductor L and transistor Q_1.
- (*) mode 2 begins when transistor Q_1 is switched off at $t=t$. The current which was flowing through the transistor would now flow through L, C, load and diode D_m. The inductor current falls until transistor Q_1 is turned on again in the next cycle.

- * The energy stored in inductor L is transferred to the load.
- * The equivalent circuits for the modes of operation are shown in figure. The waveforms for voltages and currents are shown for continuous load current.

Assuming that the inductor current rises linearly from I_1 to I_2 in time t_1 ,

$$V_s = L \frac{(I_2 - I_1)}{t_1} = L \frac{\Delta I}{t_1} \Rightarrow t_1 = \frac{\Delta I L}{V_s}$$

and the inductor current falls linearly from I_2 to I_1 in time t_2 .

$$V_s - V_a = -L \frac{\Delta I}{t_2} \Rightarrow t_2 = \frac{\Delta I L}{(V_a - V_s)}$$

where $\Delta I = I_2 - I_1$ is the peak-to-peak ripple current of inductor L.

$$\therefore \Delta I = \frac{V_s t_1}{L} = \frac{(V_a - V_s) t_2}{L}$$

Substituting $t_1 = KT$ and $t_2 = (1-K)T$ yields avg op voltage

$$V_a = V_s \frac{T}{t_2} = \frac{V_s}{1-K}$$

$$\therefore \frac{t_2}{T} = (1-K) \Rightarrow \frac{1}{f_{avg}} = \frac{1}{1-K}$$

$$\therefore (1-K) = \frac{V_s}{V_a}$$

$$\text{Substituting } k = t_1/T = f t_1, \quad t_1 = \frac{(V_a - V_s)}{V_a f}$$

- * Assuming a lossless circuit, $V_s I_s = V_a I_a = \frac{V_s I_a}{(1-K)}$ and the average input current is,

$$I_s = \frac{I_a}{1-K}$$

- * The switching period T can be found from

$$T = \frac{1}{f} = t_1 + t_2 = \frac{\Delta I L}{V_s} + \frac{\Delta I L}{(V_a - V_s)} = \frac{\Delta I L V_a}{V_s (V_a - V_s)}$$

$$\therefore \text{peak to peak ripple current } \Delta I = \frac{V_s (V_a - V_s)}{f L V_a} = \frac{V_s k}{f L V_a}$$

When the transistor is on, the capacitor supplies the load current for $t = t_1$. The average capacitor current during time t_1 is $I_c = I_a$ and the peak-to-peak ripple voltage of the capacitor is

$$\Delta V_c = V_c - V_c(t=0) = \frac{1}{c} \int_0^{t_1} I_c dt = \frac{1}{c} \int_0^{t_1} I_a dt = \frac{I_a t_1}{c}$$

$$\text{Substituting } t_1 = \frac{(V_a - V_s)}{V_a + f} , \Delta V_c = \frac{I_a (V_a - V_s)}{V_a + f c} = \frac{I_a k}{f c}$$

Condition for continuous inductor current and capacitor voltage

If I_L is the average inductor current, the inductor ripple current $\Delta I = \omega I_L$

$$\frac{K V_s}{f L} = \omega I_L = \omega I_a = \frac{\omega V_s}{(1-K)R}$$

which gives the critical value of the inductor L_c as

$$L_c = L = \frac{K(1-K)R}{\omega f}$$

If V_c is the average capacitor voltage, the capacitor ripple voltage $\Delta V_c = \omega V_a$

$$\text{W.R.T } \Delta V_c = \frac{I_a k}{f c} = \omega V_a = \omega I_a L$$

which gives the critical value of the capacitor C_c as

$$C_c = C = \frac{K}{\omega f R}$$

A boost regulator has an input voltage of $V_s = 5V$. The average output voltage $V_a = 15V$ and the average load current $I_a = 0.5A$. The switching frequency is 25kHz . If $L = 150\mu\text{H}$ and $C = 220\mu\text{F}$, determine (a) duty cycle K (b) the ripple current of inductor ΔI_L (c) the peak current of inductor I_{s1} (d) the ripple voltage of filter capacitor ΔV_C (e) critical values of L and C.

Soln : Given $V_s = 5V$, $V_a = 15V$, $f = 25\text{kHz}$, $L = 150\mu\text{H}$ and $C = 220\mu\text{F}$

$$(a) V_a = \frac{V_s}{1-K}$$

$$15 - \frac{5}{1-K} \Rightarrow K = \frac{2}{3} = 0.6667 = 66.67\%$$

$$(b) \Delta I_L = \frac{V_s(V_a - V_s)}{f L V_a} = \frac{5(15-5)}{(25K)(150\mu)(15)} = 0.89A$$

$$(c) I_s = \frac{I_a}{1-K} = \frac{0.5}{1-0.6667} = 1.5A$$

$$I_{s1} = I_s + \frac{\Delta I_L}{2} = 1.5 + \frac{0.89}{2} = 1.945A$$

$$(d) \Delta V_C = \frac{I_a R}{f C} = \frac{0.5(0.6667)}{(25K)(220\mu)} = 60.61\text{mV}$$

$$(e) R = \frac{V_a}{I_a} = \frac{15}{0.5} = 30\Omega$$

$$L_c = \frac{(1-K) K R}{2f} = \frac{(1-0.6667) 0.6667 \times 30}{2 \times 25 \times 10^3} = 133\mu\text{H}$$

$$C_c = \frac{R}{2fL} = \frac{0.6667}{2 \times 25K \times 30} = 0.44\mu\text{F}$$

Buck - Boost Regulators

- A buck boost regulator provides an output voltage that may be less than or greater than the input voltage hence the name "buck-boost". The output voltage polarity is opposite to that of the input voltage. This regulator is also known as an inverting regulator.


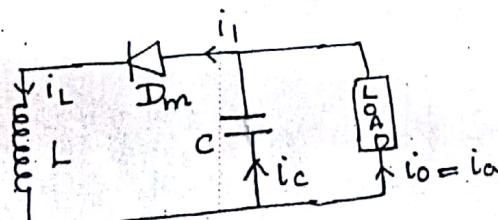
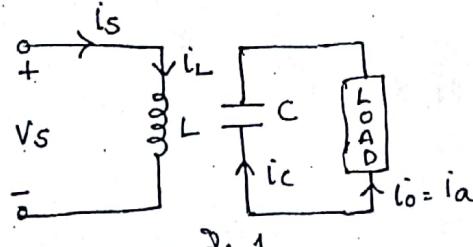
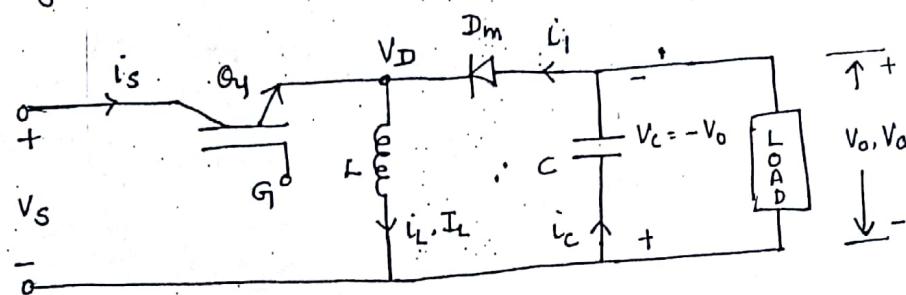


fig : Equivalent Circuits

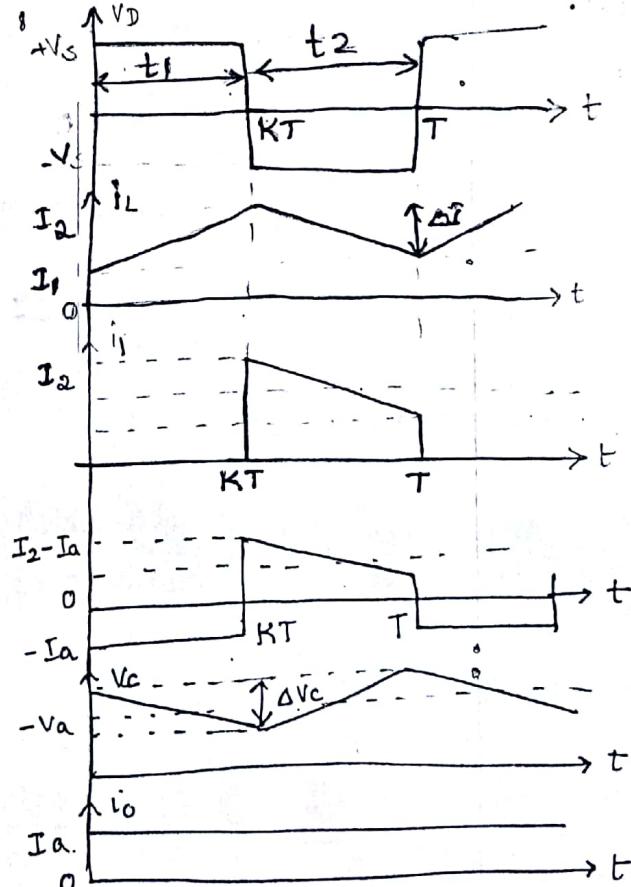

- Circuit operation can be divided into two modes.
- During mode 1, transistor Q_4 is turned on and diode D_m is reverse biased. The input current which rises flows

through inductor L and transistor Q₁.

- * During mode 2, transistor Q₁ is switched off and the current, which was flowing through inductor L, would flow through L, C, D_m, and the load.

The energy stored in inductor L would be transferred to the load and the inductor current would fall until transistor Q₁ is switched on again in the next cycle.

- * The equivalent circuits for the modes are shown in fig. and waveforms for steady state voltages and currents of the buck boost regulator are shown for a continuous load current.

Assuming that the inductor current rises linearly from I₁ to I₂ in time t₁,

$$V_s = L \frac{I_2 - I_1}{t_1} = L \frac{\Delta I}{t_1} \Rightarrow t_1 = \frac{\Delta I L}{V_s}$$

and the inductor current falls linearly from I₂ to I₁ in t₂

$$\text{i.e. } V_a = -L \frac{\Delta I}{t_2} \Rightarrow t_2 = -\frac{\Delta I L}{V_a}$$

$$\therefore \Delta I = \frac{V_s t_1}{L} = -\frac{V_a t_2}{L}$$

Substituting t₁ = kT and t₂ = (1-k)T

$$V_a = -\frac{V_s k}{(1-k)}$$

$$V_a = -\frac{V_s \cdot I_s}{I_a} = -\frac{V_s \cdot I_a k}{I_a (1-k)}$$

Assuming a lossless circuit, V_s & I_s = -V_a I_a = V_s I_a^k / (1-k)

and the average input current I_s is related to the average output current I_a by

$$I_s = \frac{I_a k}{1-k}$$

The switching period T can be found from

$$T = \frac{1}{f} = t_1 + t_2 = \frac{\Delta I L}{V_s} - \frac{\Delta I L}{V_a} = \frac{\Delta I L (V_a - V_s)}{V_s \cdot V_a}$$

and this gives the peak to peak ripple current,

$$\Delta I = \frac{V_s V_a}{f L (V_a - V_s)} \quad \text{or} \quad \Delta I = \frac{V_s K}{f L} :$$

When transistor Q_1 is on, the filter capacitor supplies the load current for $t = t_1$. The average discharging current of the capacitor is $I_c = I_a$ and the peak to peak ripple voltage of the capacitor is

$$\Delta V_c = \frac{1}{C} \int_0^{t_1} I_c dt = \frac{1}{C} \int_0^{t_1} I_a dt = \frac{I_a t_1}{C}$$

$$\text{when } t_1 = \frac{V_a}{(V_a - V_s) f}, \quad \Delta V_c = \frac{I_a V_a}{(V_a - V_s) f C} \quad \text{or} \quad \Delta V_c = \frac{I_a K}{f C}$$

A buck-boost regulator provides output voltage polarity reversal without a transformer. It has high efficiency. Under a fault condition of the transistor, the dI/dt of the fault current is limited by the inductor L and will be V_s/L . Output short-circuit protection would be easy to implement.

Condition for continuous inductor current and capacitor voltage.

If I_L is the avg. inductor current, the inductor ripple current $\Delta I = 2I_L$.

$$\frac{K V_s}{f L} = 2I_L = 2I_a = \frac{2 K V_s}{(1-K) R}$$

$$I_a = \frac{V_a}{R} = \frac{V_s \cdot K}{(1-K) R}$$

which gives the critical value of the inductor L_c as

$$L_c = L = \frac{(1-K) R}{2f}$$

If V_c is the avg. capacitor voltage, the capacitor ripple voltage $\Delta V_c = 2V_a$ $\therefore \frac{I_a K}{C f} = 2V_a = 2I_a R$

$$\frac{K}{f \cdot R} = C_c$$

which gives the critical value of the capacitor C as

$$C_c = C = \frac{K}{2fR}$$

Problem

The buck boost regulator in figure has an input voltage of $V_s = 12V$. The duty cycle $K = 0.25$ and the switching frequency is 25 KHz . The inductance $L = 150\mu\text{H}$ and filter capacitance $C = 220\mu\text{F}$. The average load current $I_a = 1.25\text{ A}$. Determine

- (a) the average output voltage V_a
- (b) peak to peak output voltage ripple ΔV_c
- (c) peak to peak ripple current of inductor ΔI
- (d) peak current of the transistor I_p
- (e) the critical values of L and C .

Soln Given $V_s = 12V$, $K = 0.25$, $I_a = 1.25\text{ A}$, $f = 25\text{ KHz}$, $L = 150\mu\text{H}$ and $C = 220\mu\text{F}$.

$$(a) V_a = \frac{-V_s(K)}{(1-K)} = \frac{-12(0.25)}{(1-0.25)} = -4V$$

$$(b) \Delta V_c = \frac{I_a K}{f L} = \frac{1.25 \times 0.25}{25K(220\mu)} = 56.8\text{ mV}$$

$$(c) \Delta I = \frac{V_s K}{f L} = \frac{12(0.25)}{25K(150\mu)} = 0.8A$$

(d) $I_s = \frac{I_a K}{1-K} = 0.4167\text{ A}$. Because I_s is the average of duration KT , the peak-to-peak current of the transistor

$$I_p = \frac{I_s}{K} + \frac{\Delta I}{2} = \frac{0.4167}{0.25} + \frac{0.8}{2} = 2.067\text{ A}$$

$$(e) R = \frac{-V_a}{I_a} = \frac{4}{1.25} = 3.2\Omega$$

$$L_c = \frac{(1-K)R}{2f} = \frac{(1-0.25)3.2}{2 \times 25 \times 10^3} = 450\mu\text{H}$$

$$C_c = \frac{K}{2fR} = \frac{0.25}{2 \times 25 \times 10^3 \times 3.2} = 1.56\mu\text{F}$$